

## ADC/DAC

### Objectives

To study another group of analog IC circuits of great importance, data converters.

### Overview

#### 1. Ideal D/A Converter, DAC

Consider the block diagram of an N-bit D/A converter shown in Fig. 1. Here  $B_{in}$  is defined to be an N-bit digital signal (or word) such that

$$B_{in} = b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N} \quad (7.1)$$

where  $b_i$  equals 1 or 0 (i.e.,  $b_i$  is a binary digit).

 


Fig. 1 A block diagram representing a D/A converter.

We also define  $b_1$  as the most significant bit (MSB) and  $b_N$  as the least significant bit (LSB). Furthermore, we have assumed here that  $B_{in}$  represents a positive value, resulting in a unipolar D/A converter. A *unipolar D/A converter* produces an output signal of only one polarity.

The analog output signal,  $V_{out}$ , is related to the digital signal,  $B_{in}$ , through an analog reference signal,  $V_{ref}$ . For simplicity, we assume that both  $V_{out}$  and  $V_{ref}$  are voltage signals, although, in general, they may be other physical quantities, such as current or charge. The relationship between these three signals for a unipolar D/A converter is given by

$$V_{out} = V_{ref}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}) = V_{ref} B_{in} \quad (7.2)$$

It is useful to define  $V_{\text{LSB}}$  to be the voltage change when one LSB changes, or, mathematically,

$$V_{\text{LSB}} \equiv \frac{V_{\text{ref}}}{2^N} \quad (7.3)$$

Also useful (particularly in measuring errors) is the definition of a new “unit,” namely, LSB units, which are in fact unitless.

$$1 \text{ LSB} = \frac{1}{2^N} \quad (7.4)$$

The transfer curve for an ideal 2-bit D/A converter is shown in Fig. 2. Note that, although only a finite number of analog values occur at the output, for an ideal D/A converter, the output signals are well-defined values. Also note that the maximum value of  $V_{\text{out}}$  is not  $V_{\text{ref}}$  but rather  $V_{\text{ref}}(1-2^{-N})$ , or equivalently,  $V_{\text{ref}} - V_{\text{LSB}}$ .

 


Fig. 2 Input-output transfer curve for an ideal 2-bit D/A converter.

Finally, as we can see from (7.2), a multiplying D/A converter is realized by simply allowing the reference signal,  $V_{\text{ref}}$ , to be a varying input signal along with the digital input,  $B_{\text{in}}$ . Such an arrangement results in  $V_{\text{out}}$  being proportional to the multiplication of the input signals,  $B_{\text{in}}$  and  $V_{\text{ref}}$ .

## 2. Ideal Analog/Digital Converter, ADC

The block diagram representation for an A/D converter is shown in Fig. 3, where  $B_{\text{out}}$  is the digital output word while  $V_{\text{in}}$  and  $V_{\text{ref}}$  are the analog input and reference signals, respectively. Also, we define  $V_{\text{LSB}}$  to be the signal change corresponding to a single LSB changes as in the D/A case.

 


Fig. 3 A block diagram representing a D/A converter.

For an A/D converter, the following equation relates these signals,

$$V_{\text{ref}}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_N 2^{-N}) = V_{\text{in}} \pm V_x \quad (7.5)$$

where

$$-\frac{1}{2}V_{\text{LSB}} \leq V_x \leq \frac{1}{2}V_{\text{LSB}} \quad (7.6)$$

Note that there is now a range of valid input values that produce the same digital output word. This signal ambiguity produces what is known as *quantization error*. Also, note that no quantization error occurs in the case of a D/A converter since the output signals are well defined.

 


Fig. 4 Input-Output transfer curve for a 2-bit A/D converter.

Of course, quantization errors will occur if a 6-bit D/A converter is used to convert a 10-bit digital signal, but in this case, the quantization error occurs in the conversion from a 10-bit digital signal to a 6-bit digital signal.

A transfer curve for an A/D converter can be sketched as shown in Fig. 4 for a 2-bit converter. Note that the transitions along the  $V_{in}$  axis are offset by  $1/2V_{LSB}$ , so that the midpoints of the staircase curve fall precisely on the equivalent D/A converter curve.

Here, we define the transition voltage at  $V_{ij}$ , where the subscript  $ij$  indicates the upper Bout value of the transition. For example,  $V_{01}$  is shown in Fig. 4 as the voltage (normalized with respect to  $V_{ref}$ ) for the transition from 00 to 01.

Finally, it should be noted that the relation shown in (7.6) holds only if the input signal remains within 1 LSB of the two last transition voltages. Specifically, for the 2-bit transfer curve shown in Fig. 4,  $V_{in}$  should remain less than  $7/8 V_{ref}$  and greater than  $-1/8 V_{ref}$ . Otherwise, the quantizer is said to be *overloaded* since the magnitude of the quantization error would be larger than  $V_{LSB}/2$ .

### 3. Quantization Noise

As mentioned in section 2, quantization errors occur even in ideal A/D converters. In this section, we model these errors as being equivalent to an additive noise source and then find the power of this noise source.

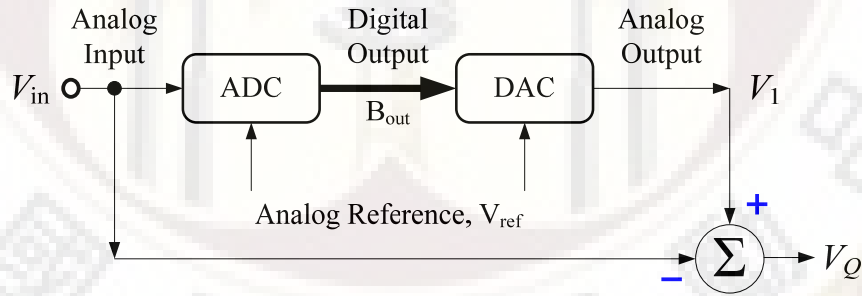


Fig. 5 A circuit to investigate quantization noise behavior

Consider the setup shown in Fig. 5, where both N-bit converters are ideal. Since we have

$$V_Q = V_1 - V_{in} \quad (7.7)$$

we can rearrange this equation as

$$V_1 = V_Q + V_{in} \quad (7.8)$$

Although this rearrangement is trivial, it has important implications because (7.8) shows that the quantized signal,  $V_1$ , can be modelled as the input signal,  $V_{in}$ ,

plus some additive quantization noise signal,  $V_Q$ .

Note that (7.8) is exact because no approximations have been made here. The quantization noise modelling becomes approximate once some assumptions are made about the statistical properties of  $V_Q$ .

#### 4. Resolution

The *resolution* of a converter is defined to be the number of distinct analog levels corresponding to the different digital words. Thus, an  $N$ -bit resolution implies that the converter can resolve  $2^N$  distinct analog levels. Resolution is not necessarily an indication of the accuracy of the converter, but instead it usually refers to the number of digital input or output bits.

#### 5. Offset

In a D/A converter, the *offset error*,  $E_{\text{off}}$ , is defined to be the output that occurs for the input code that should produce zero output, or mathematically,

$$E_{\text{off(D/A)}} = \left. \frac{V_{\text{out}}}{V_{\text{LSB}}} \right|_{0\dots 0}$$

where the offset error is in units of LSBs.

Similarly, for an A/D converter, the offset error is defined as the deviation of  $V_{0\dots 01}$  from  $1/2 V_{\text{LSB}}$ , or mathematically,

$$E_{\text{off(A/D)}} = \frac{V_{0\dots 01}}{V_{\text{LSB}}} - \frac{1}{2} \text{LSB}$$

#### 6. Gain Error

The *gain error* is defined to be the difference at the full-scale value between the ideal and actual curves when the offset error has been reduced to zero.

For a D/A converter, the gain error,  $E_{\text{gain(D/A)}}$ , in units of LSBs, is given by

$$E_{\text{gain(D/A)}} = \left( \left. \frac{V_{\text{out}}}{V_{\text{LSB}}} \right|_{1\dots 1} - \left. \frac{V_{\text{out}}}{V_{\text{LSB}}} \right|_{0\dots 0} \right) - (2^N - 1)$$

Similarly, for an A/D converter, the equivalent gain error,  $E_{\text{gain(A/D)}}$ , in units of LSBs, is given by

$$E_{\text{gain(A/D)}} = \left( \frac{V_{1\dots 1}}{V_{\text{LSB}}} - \frac{V_{0\dots 1}}{V_{\text{LSB}}} \right) - (2^N - 2)$$

Graphically illustrations of gain and offset errors are shown in Fig. 5

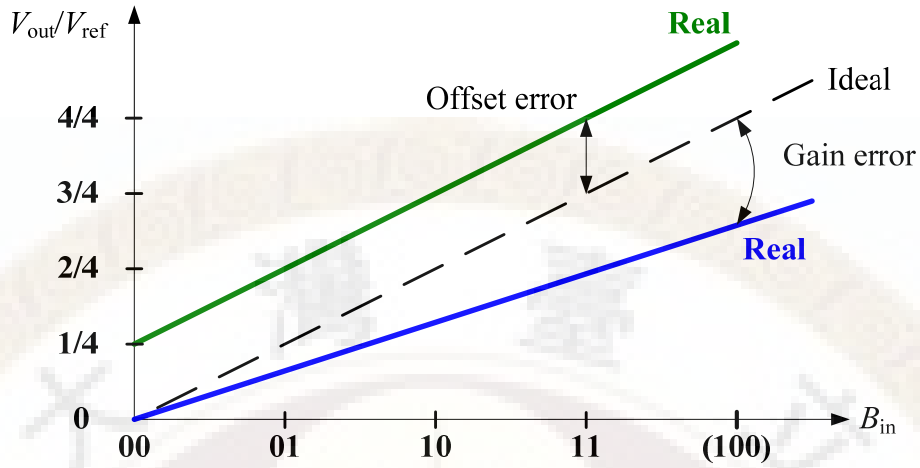


Fig. 5 Illustrating offset and gain errors for a 2-bit D/A converter

## 7. Accuracy and Linearity

The *absolute accuracy* of a converter is defined to be the difference between the expected and actual transfer responses. The absolute accuracy includes the offset, gain, and linearity errors.

The term relative accuracy is sometimes used and is defined to be the accuracy after the offset and gain errors have been removed. It is also referred to as the *maximum integral nonlinearity error* (described later) and we will refer to it as such.

Accuracy can be expected as a percentage error of full-scale value, as the effective number of bits, or as a fraction of a LSB. For example, a 12-bit accuracy implies that the converter's error is less than the full-scale value divided by  $2^{12}$ .

## 8. Linearity

### Integral Nonlinearity (INL) Error

After both the offset and gain errors have been removed, the integral nonlinearity (INL) error is defined to be the deviation from a straight line. However, what straight line should be used? A conservative measure of nonlinearity is to use the endpoints of the converter's transfer response to define the straight line.

An alternative definition is to find the best-fit straight line such that the maximum difference (or perhaps the mean squared error) is minimized.

These two definitions are illustrated in Fig. 6. One should be aware that, we define INL values for each digital word (and thus these values can be plotted for a

single converter), whereas others sometimes define the term “INL” as the maximum magnitude of the INL values (or equivalently, as the relative accuracy).

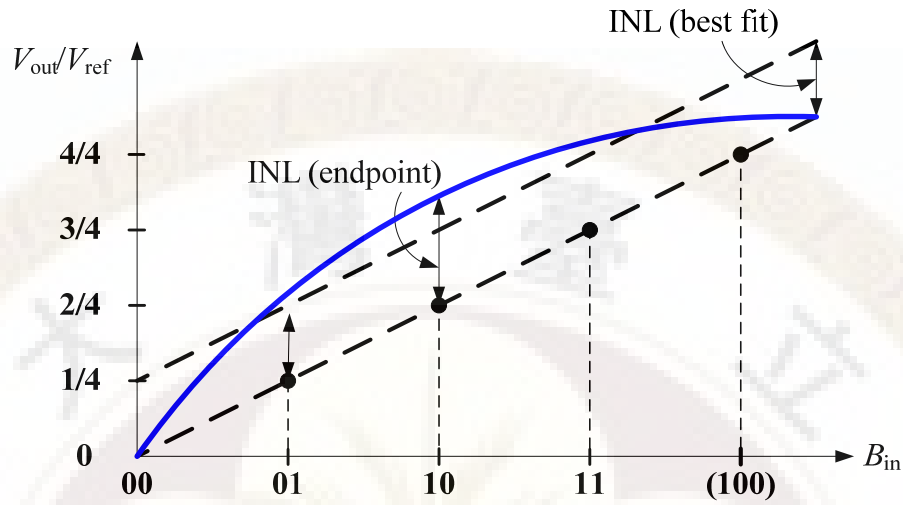


Fig. 6 Integral Nonlinear (INL) Error in a 2-bit D/A converter

Typically INL is measured by slowly sweeping the converter input over its full-scale range; hence it is a measure of the converter’s accuracy only at low input signal frequencies.

#### 9. A/D Conversion Time and Sampling Rate

In A/D converter, the *conversion time* is the time taken for the converter to complete a single measurement including acquisition time of the input signal. On the other hand, the maximum *sampling rate* is the speed at which samples can be continuously converted and is typically the inverse of the conversion time.

However, one should be aware that some converters have a large latency between the input and the output due to pipelining and multiplexing, yet they still maintain a high sampling rate. For example, a pipelined 12-bit A/D converter may have a conversion time of 2 ns (i.e., a sampling rate of 500 MHz) yet a latency from input to output of 24 ns.

#### 10. D/A Settling Time and Sampling Rate

In D/A converter, the *settling time* is defined as the time it takes for the converter to settle to within some specified amount of the final value (usually 0.5 LSB). The *sampling rate* is the rate at which samples can be continuously converted and is typically the inverse of the settling time.



## Instrument Requirement

| Instrument   | Quantity | Components     | Quantity |
|--------------|----------|----------------|----------|
| Oscilloscope | 1        | Power supplier | 2        |
| Multi-meter  | 1        | Function Gen.  | 1        |

## Components Requirement

| Components        | Quantity | Components                            | Quantity |
|-------------------|----------|---------------------------------------|----------|
| $\mu A$ 741       | 1        | 100pF (100)                           | 1        |
| DAC 0800          | 1        | 10 k $\Omega$                         | 1        |
| ADC 0804          | 1        | 3 k $\Omega$                          | 2        |
| 0.1 $\mu F$ (104) | 2        | VR (10 k $\Omega$ )                   | 1        |
| 10 $\mu F$        | 2        | LEDs                                  | 8        |
| 50 pF (50)        | 1        | 1.2 k $\Omega$ (or 330~500 $\Omega$ ) | 8        |


## Instrument confirmation

Before you proceed to any part of the experiment, please remember to do the **Instrument Examinations** to the instruments before performing any experiment. The examining procedures are shown in experiment 1.

## Components confirmation

### 1. PINOUT Diagram


ADC080X  
Dual-In-Line and Small Outline (SO) Packages

 

DS005871-30

ADC0804

Dual-In-Line Package

 


DS005686-13

DAC0800



## 2. Functional confirmation of LED

Check 1.

 


$$- R_{RB} (\text{逆偏電阻}) +$$

$$+ R_{FB} (\text{順偏電阻}) -$$


$$R_{FB} (\sim M\Omega) \ll R_{RB} (O.L.)$$

Check 2.

 

※ **Note:** Please do not directly provide DC power with LED. Otherwise it will be easily damaged.
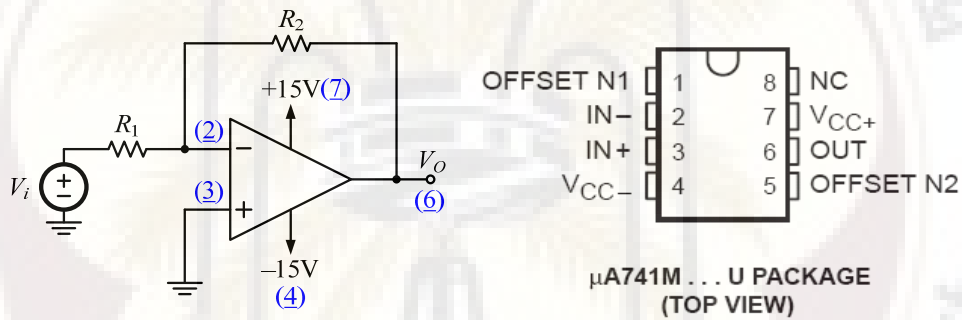
## 3. $\mu A741$ – PINOUT & Functional confirmation



$$\text{Check 1. } A_v = \frac{V_o}{V_i} = - \left( \frac{R_2}{R_1} \right)$$

$$\text{Check 2. } f_{3dB} = 100kHz \sim 500kHz$$

※ **Note:** Recall the expression of gain – bandwidth product:  $A_v \times f_{3dB} = \text{constant}$ , that is,  $f_{3dB}$  will reduce as  $A_v$  increases. If the results of confirmation appear the same as those shown in check 1 and 2, the  $\mu A741$  chip of OP amp is workable.

## Lab Work

### 1. ADC0804 Testing circuit

 


Fig. 1 ADC0804 Testing circuit

*Note:* If the LEDs are not easy to visualize, try to change the current limited resistance  $1.2\text{ k}\Omega$  to the values from  $330\text{ }\Omega$ ~  $500\text{ }\Omega$ .

### 2. Rest ADC0804

- (1) In Fig. 1, SW open. (i.e., do not connect pin 3 and pin 5 to ground.)
- (2) Supply voltage  $V_{CC} = +5\text{V}$ .
- (3) At step (2), all the LEDs or part of the 8-LED will turn ON. (亮)
- (4) SW close in a short period (i.e., reset the ADC0804 chip for a second).
- (5) SW open. (i.e., disconnect pin 3 and pin 5 from ground.)
- (6) At step (5), all the LEDs will turn OFF. (暗).

### 3. Measure the voltage as full load. (No need to perform)

- (1) Supply voltage signal  $V_{in} = 0\text{V}$ , and  $V_R$ .
- (2) Slowly increase  $V_R$  from  $2.5\text{V}$  to  $5\text{V}$ .
- (3) Observe whether the digital output (LEDs) can mutually radiate. If they are not so, try to change a new ADC0804 chip.
- (4) Adjust  $V_R$  as the digital output just equals to 1111-1111.

(5) Record  $V_R =$  \_\_\_\_\_ V.

4. Measure Analog voltage value to Digital output

(1) Set  $V_R = +2.5\text{V}$  and  $V_{in} = 0 \sim 2.5\text{V}$ .

(2) Slowly increase  $V_{in}$  from 0 to 5V, and record the  $V_{in}$  by using the multimeter with the corresponding output in the following table.

(3) Maintain the circuit in breadboard, and do not disconnect or unplug any devices.

| Analog input $V_{in}$ (V)<br>(Use Multimeter) | Digital output (Binary) | Digital output (Decimal) |
|---|-------------------------|--------------------------|
|   | 0000 0001               | 1                        |
|   | 0000 0010               | 2                        |
|   | 0000 0100               | 4                        |
|   | 0000 1000               | 8                        |
|   | 0001 0000               | 16                       |
|   | 0010 0000               | 32                       |
|   | 0100 0000               | 64                       |
|   | 1000 0000               | 128                      |

※ *Homework #1:* Apply the measured data from the above table in the editing software such as EXCEL and MATLAB, and plot the diagram of decimal digital output versus analog input.

## 5. DAC0800 Testing circuit

 


Fig. 2 DAC0800 Testing circuit

- (1) In Fig. 2, supply  $V_{DD} = +5V$ ,  $V_{ref} = +5V$  for DAC circuit and  $V_+ = +15V$ ,  $V_- = -15V$  for  $\mu A741$  OP Amp.
- (2) Input 1111-1111 to the digital input terminals.  
(Hint: In the circuit, Logic 1 = +5V, Logic 0 = 0V.)
- (3) Adjust VR 10 k $\Omega$ , use multi-meter  $\blacktriangleright V_{out}$  changed ? (Y/N)  $\blacktriangleright$  If  $V_{out}$  is not changed, try to trouble shoot the circuit in the breadboard.
- (4) Carefully adjust VR 10 k $\Omega$  to have  $V_{out} = +5V$ .
- (5) Record the value of VR = \_\_\_\_\_ k $\Omega$ .
- (6) Refer to the following table and change the digital input.
- (7) Record the  $V_{out}$  by using the multimeter in the following table.
- (8) Maintain the circuit in breadboard, and do not disconnect, unplug or adjust any devices.

| Digital iutput (Binary) | Digital iutput (Decimal)(V) | Analog output $V_{out}$ (V)<br>(Use Multimeter) |
|-------------------------|-----------------------------|---|
| 0000 0001               | 1                           |   |
| 0000 0010               | 2                           |   |
| 0000 0100               | 4                           |   |
| 0000 1000               | 8                           |   |
| 0001 0000               | 16                          |   |
| 0010 0000               | 32                          |   |
| 0100 0000               | 64                          |   |
| 1000 0000               | 128                         |   |

※ *Homework #2:* Apply the measured data from the above table in the editing software such as EXCEL and MATLAB, and plot the diagram of decimal digital input versus analog output.

## 6. Connection of Fig. 1 + Fig. 2

 


Fig. 1 ADC0804 Testing circuit

 


Fig. 2 DAC0800 Testing circuit

- (1) Connect DB7(MSB) in ADC0804 test circuit to B1(MSB) in DAC0800 test circuit, DB6 to B2 ... ,and DB0(LSB) to B8(LSB), respectively.
- (2) Short the ground in Fig. 1 and Fig. 2 with each other.
- (3) Do not unplug the current limited resistance 1.2 kΩ and the LEDs in ADC0804 testing circuit.

## 7. Rest ADC0804

- (4) In Fig. 1, SW open. (i.e., do not connect pin 3 and pin 5 to ground.)
- (5) In Fig. 1, supply voltage  $V_{CC} = +5V$ .
- (6) SW close in a short period (i.e., reset the ADC0804 chip for a second).
- (7) SW open. (i.e., disconnect pin 3 and pin 5 from ground.)

## 8. Measure Analog voltage $V_{in}$ to $V_{out}$

- (8) In Fig. 1, supply voltage  $V_R = +2.5V$ .
- (9) Slowly increase  $V_{in}$  from 0 to 5V just as the LEDs are sparked as the following table. Record  $V_{in}$  and  $V_{out}$  by using the same multimeter and fill up the following table.

| Analog input $V_{in}$<br>(use the same meter) | Digital output<br>(Binary) | Analog output $V_{out}$<br>(use the same meter) | Quantization Error,<br>$V_Q = V_{out} - V_{in}$ |
|---|----------------------------|---|---|
|   | 0000 0001                  |   |   |
|   | 0000 0010                  |   |   |
|   | 0000 0100                  |   |   |
|   | 0000 1000                  |   |   |
|   | 0001 0000                  |   |   |
|   | 0010 0000                  |   |   |
|   | 0100 0000                  |   |   |
|   | 1000 0000                  |   |   |

✂ *Homework #3*: Apply the measured data from the above table in the editing software such as EXCEL and MATLAB, and plot the diagram of  $V_Q$  vs  $V_{in}$  and verify what type of the quantization error had occurred in your circuit.

## Reference

1. A.S. Sedra and K.C. Smith, *Microelectronic Circuits*, 6<sup>th</sup> ed., Oxford University Press publishing, New York, 2011.
2. A.S. Sedra and K.C. Smith, *Laboratory Manual for Microelectronic Circuits*, 3<sup>rd</sup> ed., Oxford University Press publishing, New York, 1997.
3. Paul Horowitz, Winfield Hill, *The art of electronics*, 2<sup>nd</sup> ed., Cambridge University Press, New York, 1989.
4. Paul R. Gray, Paul J. Hurst, Stephen H. Lewis, Robert G. Meyer (Author), *Analysis and Design of Analog Integrated Circuits*, 5<sup>th</sup> ed., Wiley, January 20, 2009.
5. Tony Chan Carusone, David Johns, Kenneth W. Martin, *Analog Integrated Circuit Design*, 2<sup>nd</sup> International student edition, John Wiley & Sons, April 23, 2012.