

## Oscillators

### Objectives

Be familiar with the *Barkhausen criterion* and various kinds of oscillators.

### Overview

#### 1. The Wien-Bridge Oscillator

One of the simplest sinusoidal oscillator circuits is based on the Wien-bridge. Fig. 1 shows a Wien-bridge oscillator without the nonlinear gain-control network. The circuit consists of an op amp

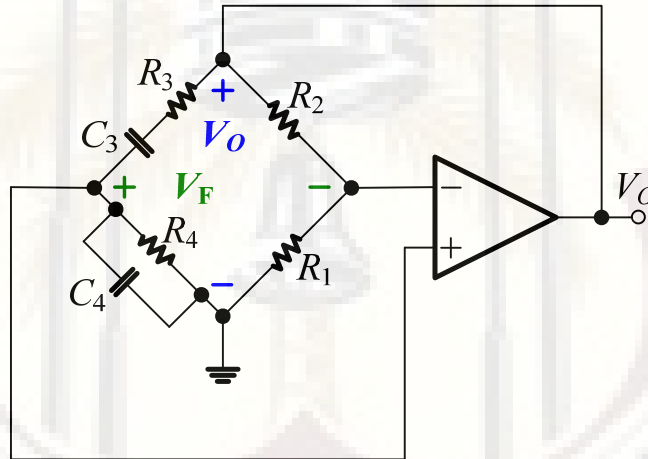


Fig. 1 A Wien-bridge oscillator without amplitude stabilization

$$V_F = V_O \times \frac{R_4 // \frac{1}{sC_4}}{\left(R_3 + \frac{1}{sC_3}\right) + \left(R_4 // \frac{1}{sC_4}\right)} - V_O \times \frac{R_1}{R_1 + R_2}$$

$$\beta = \frac{V_F}{V_O} = \frac{R_4 // \frac{1}{sC_4}}{\left(R_3 + \frac{1}{sC_3}\right) + \left(R_4 // \frac{1}{sC_4}\right)} - \frac{R_1}{R_1 + R_2}$$

$$\begin{aligned}
\beta(s) &= \frac{V_F}{V_O} = \frac{\frac{1}{\frac{1}{R_4} + sC_4}}{\left(R_3 + \frac{1}{sC_3}\right) + \left(\frac{1}{\frac{1}{R_4} + sC_4}\right)} - \frac{R_1}{R_1 + R_2} \\
&= \frac{1}{1 + \left(R_3 + \frac{1}{sC_3}\right) \cdot \left(\frac{1}{R_4} + sC_4\right)} - \frac{R_1}{R_1 + R_2} \\
\beta(s) &= \frac{1}{1 + \frac{R_3}{R_4} + \frac{C_4}{C_3} + s \cdot \left(R_3C_4 + \frac{1}{R_4C_3}\right)} - \frac{R_1}{R_1 + R_2} \\
\beta(j\omega) &= \frac{1}{1 + \frac{R_3}{R_4} + \frac{C_4}{C_3} + j \cdot \left(\omega R_3C_4 - \frac{1}{\omega R_4C_3}\right)} - \frac{R_1}{R_1 + R_2} \\
&= \frac{1}{3 + j \cdot \left(\omega R_3C_4 - \frac{1}{\omega R_4C_3}\right)} - \frac{R_1}{R_1 + R_2}
\end{aligned}$$

The loop gain will be a real number. Therefore, assume the imaginary part of denominator of  $\beta(j\omega)$  equals 0, and  $R_3 = R_4 = C_3 = C_4 = C$ , we have

$$\omega_0 = \frac{1}{\sqrt{R_3R_4C_3C_4}} = \frac{1}{RC}$$

To oscillate the circuit, the **Barkhausen criterion** should be satisfied only at one frequency ( $\omega_0$ ), that is,


$$\begin{aligned}
A(j\omega_0)\beta(j\omega_0) &= 1 \\
\because A(j\omega_0) &\approx \infty \rightarrow \beta(j\omega_0) = 0 = \frac{1}{3} - \frac{R_1}{R_1 + R_2} \\
\rightarrow \frac{R_1}{R_1 + R_2} &= \frac{1}{3} \rightarrow 3R_1 = R_1 + R_2 \rightarrow 2R_1 = R_2
\end{aligned}$$

The condition of oscillations at  $\omega_0$  is,


$$\frac{R_2}{R_1} = \frac{\text{橋上電阻}}{\text{橋下電阻}} = 2$$

To ensure that oscillations will start, one chooses  $R_2/R_1$  slightly greater than 2.

## 2. Phase-Shift Oscillator

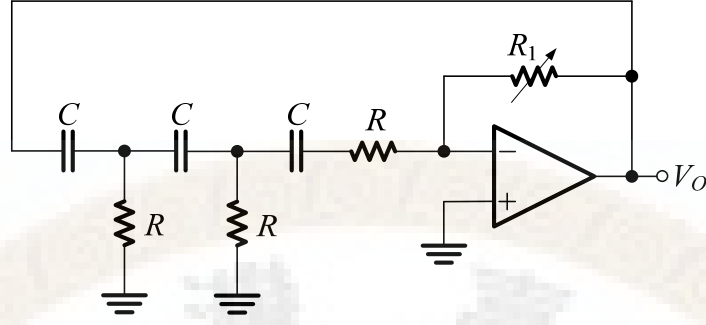

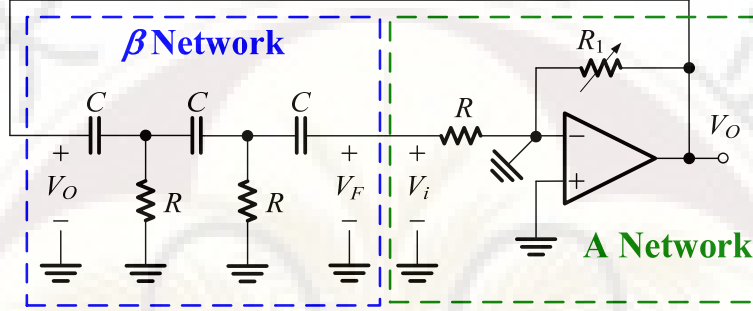The A-network and  $\beta$ -network is shown as follow



$$A = \frac{V_O}{V_i} = -\frac{R_1}{R}$$

$$V_F = V_O \times \frac{\left[ \left( (R + Z_C) \parallel R \right) + Z_C \right] \parallel R}{\left\{ \left[ \left( (R + Z_C) \parallel R \right) + Z_C \right] \parallel R \right\} + Z_C} \times \frac{(R + Z_C) \parallel R}{\left( (R + Z_C) \parallel R \right) + Z_C} \times \frac{R}{R + Z_C}$$

$$\beta = \frac{V_F}{V_O} = \frac{\left[ \left( \left( R + \frac{1}{sC} \right) \parallel R \right) + \frac{1}{sC} \right] \parallel R}{\left\{ \left[ \left( R + \frac{1}{sC} \right) \parallel R + \frac{1}{sC} \right] \parallel R \right\} + \frac{1}{sC}} \times \frac{\left( R + \frac{1}{sC} \right) \parallel R}{\left[ \left( R + \frac{1}{sC} \right) \parallel R \right] + \frac{1}{sC}} \times \frac{sCR}{sCR + 1} = (1) \times (2) \times (3)$$

where:

$$R + \frac{1}{sC} = \frac{1 + sCR}{sC}, \left( R + \frac{1}{sC} \right) \parallel R = \frac{1}{\frac{sC}{1 + sCR} + \frac{1}{R}} = \frac{(1 + sCR)R}{sCR + 1 + sCR} = \frac{R + sCR^2}{1 + s2CR}$$

$$\left( R + \frac{1}{sC} \right) \parallel R + \frac{1}{sC} = \frac{R + sCR^2}{1 + s2CR} + \frac{1}{sC} = \frac{sC(R + sCR^2) + 1 + s2CR}{sC(1 + s2CR)} = \frac{s^2C^2R^2 + s3CR + 1}{sC + s^22C^2R}$$

$$\left[ \left( R + \frac{1}{sC} \right) \parallel R + \frac{1}{sC} \right] \parallel R = \left( \frac{1}{R} + \frac{sC + s^22C^2R}{s^2C^2R^2 + s3CR + 1} \right)^{-1}$$

$$= \left( \frac{s^2C^2R^2 + s3CR + 1 + R(sC + s^22C^2R)}{R(s^2C^2R^2 + s3CR + 1)} \right)^{-1} = \frac{R(s^2C^2R^2 + s3CR + 1)}{s^2C^2R^2 + s3CR + 1 + R(sC + s^22C^2R)}$$

$$= \frac{R(s^2C^2R^2 + s3CR + 1)}{s^2C^2R^2 + s3CR + 1 + sCR + s^22C^2R^2} = \frac{s^2C^2R^3 + s3CR^2 + R}{s^23C^2R^2 + s4CR + 1}$$

$$\begin{aligned}
(1) \quad & \frac{\left[ \left( \left( R + \frac{1}{sC} \right) // R \right) + \frac{1}{sC} \right] // R}{\left\{ \left[ \left( R + \frac{1}{sC} \right) // R + \frac{1}{sC} \right] // R \right\} + \frac{1}{sC}} = \frac{\frac{s^2 C^2 R^3 + s 3 C R^2 + R}{s^2 3 C^2 R^2 + s 4 C R + 1}}{\frac{s^2 C^2 R^3 + s 3 C R^2 + R}{s^2 3 C^2 R^2 + s 4 C R + 1} + \frac{1}{sC}} \\
&= \frac{\frac{s^2 C^2 R^3 + s 3 C R^2 + R}{s^2 3 C^2 R^2 + s 4 C R + 1}}{sC \left( \frac{s^2 C^2 R^3 + s 3 C R^2 + R}{s^2 3 C^2 R^2 + s 4 C R + 1} \right) + \frac{1}{sC}} \\
&= \frac{sC \left( \frac{s^2 C^2 R^3 + s 3 C R^2 + R}{s^2 3 C^2 R^2 + s 4 C R + 1} \right)}{sC \left( \frac{s^2 C^2 R^3 + s 3 C R^2 + R}{s^2 3 C^2 R^2 + s 4 C R + 1} \right) + \frac{1}{sC}} \\
&= \frac{s^3 C^3 R^3 + s^2 3 C^2 R^2 + s C R}{s^3 C^3 R^3 + s^2 3 C^2 R^2 + s C R + s^2 3 C^2 R^2 + s 4 C R + 1} \\
&= \frac{s^3 C^3 R^3 + s^2 3 C^2 R^2 + s C R}{s^3 C^3 R^3 + s^2 6 C^2 R^2 + s 5 C R + 1} = \frac{s^3 + s^2 \left( \frac{3}{C R} \right) + s \left( \frac{1}{C^2 R^2} \right)}{s^3 + s^2 \left( \frac{6}{C R} \right) + s \left( \frac{5}{C^2 R^2} \right) + \left( \frac{1}{C^3 R^3} \right)} \\
(2) \quad & \frac{\left( R + \frac{1}{sC} \right) // R}{\left[ \left( R + \frac{1}{sC} \right) // R \right] + \frac{1}{sC}} = \frac{\frac{R + s C R^2}{1 + s 2 C R}}{\frac{R + s C R^2}{1 + s 2 C R} + \frac{1}{sC}} = \frac{\frac{R + s C R^2}{1 + s 2 C R}}{\frac{sC \left( R + s C R^2 \right) + 1 + s 2 C R}{sC \left( 1 + s 2 C R \right)}} \\
&= \frac{sC \left( R + s C R^2 \right)}{sC \left( R + s C R^2 \right) + 1 + s 2 C R} = \frac{s C R + s^2 C^2 R^2}{\left( s C R + s^2 C^2 R^2 \right) + 1 + s 2 C R} = \frac{s^2 C^2 R^2 + s C R}{s^2 C^2 R^2 + s 3 C R + 1} \\
&= \frac{s^2 + s \left( \frac{1}{C R} \right)}{s^2 + s \left( \frac{3}{C R} \right) + \left( \frac{1}{C^2 R^2} \right)}; \quad (3) \quad \frac{R}{R + Z_c} = \frac{R}{R + \frac{1}{sC}} = \frac{s C R}{s C R + 1}
\end{aligned}$$

$$\begin{aligned}
\beta(s) &= \frac{V_F}{V_O} = (1) \times (2) \times (3) \\
&= \frac{s^3 + s^2 \left( \frac{3}{C R} \right) + s \left( \frac{1}{C^2 R^2} \right)}{s^3 + s^2 \left( \frac{6}{C R} \right) + s \left( \frac{5}{C^2 R^2} \right) + \left( \frac{1}{C^3 R^3} \right)} \times \frac{s^2 + s \left( \frac{1}{C R} \right)}{s^2 + s \left( \frac{3}{C R} \right) + \left( \frac{1}{C^2 R^2} \right)} \times \frac{s C R}{s C R + 1} \\
&= \frac{s \left[ s^2 + s \left( \frac{3}{C R} \right) + \left( \frac{1}{C^2 R^2} \right) \right]}{s^3 + s^2 \left( \frac{6}{C R} \right) + s \left( \frac{5}{C^2 R^2} \right) + \left( \frac{1}{C^3 R^3} \right)} \times \frac{s^2 + s \left( \frac{1}{C R} \right)}{s^2 + s \left( \frac{3}{C R} \right) + \left( \frac{1}{C^2 R^2} \right)} \times \frac{s C R}{s C R + 1}
\end{aligned}$$

$$\begin{aligned}
\rightarrow \beta(s) &= \frac{V_F}{V_O} = \frac{s^2 \left( s + \frac{1}{CR} \right)}{s^3 + s^2 \left( \frac{6}{CR} \right) + s \left( \frac{5}{C^2 R^2} \right) + \left( \frac{1}{C^3 R^3} \right)} \times \frac{s}{s + \frac{1}{CR}} \\
&= \frac{s^3}{s^3 + s^2 \left( \frac{6}{CR} \right) + s \left( \frac{5}{C^2 R^2} \right) + \left( \frac{1}{C^3 R^3} \right)} = \frac{1}{1 + \left( \frac{6}{sCR} \right) + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3}} \\
\rightarrow \beta(j\omega) &= \frac{1}{1 + \left( \frac{6}{sCR} \right) + \frac{5}{s^2 C^2 R^2} + \frac{1}{s^3 C^3 R^3}} = \frac{1}{1 + \left( \frac{6}{j\omega CR} \right) - \frac{5}{\omega^2 C^2 R^2} - \frac{1}{j\omega^3 C^3 R^3}} \\
\rightarrow \beta(j\omega) &= \frac{1}{1 - \frac{5}{\omega^2 C^2 R^2} + j \left( \frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR} \right)}
\end{aligned}$$

Physically,  $\beta(j\omega)$  = real number. Thus, we have

$$\begin{aligned}
\frac{1}{\omega^3 C^3 R^3} - \frac{6}{\omega CR} &= 0, \rightarrow \frac{1}{\omega^3 C^3 R^3} = \frac{6}{\omega CR}, \rightarrow \omega_0^2 = \frac{1}{6R^2 C^2}, \left( \text{or } \omega_0^2 R^2 C^2 = \frac{1}{6} \right) \\
\rightarrow \beta(j\omega_0) &= \frac{1}{1 - \frac{5}{\omega_0^2 C^2 R^2}} = \frac{1}{1 - 30} = -\frac{1}{29}, \therefore A = \frac{V_O}{V_i} = -\frac{R_1}{R}
\end{aligned}$$

Apply Barkhausen stability criterion, we have

$$A\beta(j\omega_0) = \left( -\frac{R_1}{R} \right) \times \left( -\frac{1}{29} \right) = 1, \rightarrow \boxed{\frac{R_1}{R} = 29}$$

### 3. Triangular waveform using bistable multivibrator

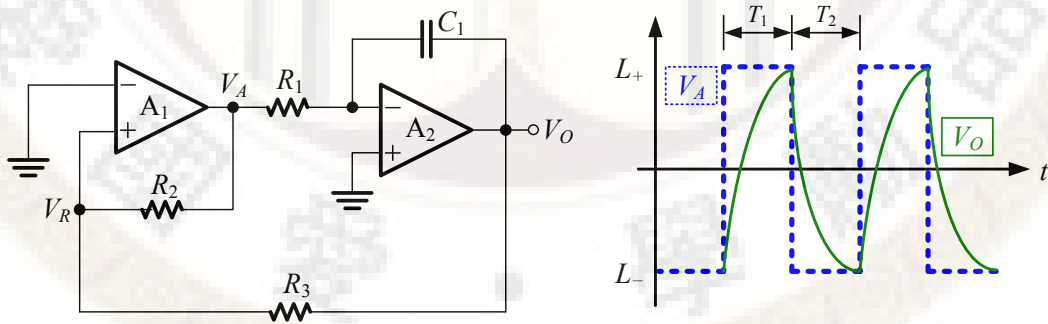


Fig. 2 Triangular waveform using bistable multivibrator

$$V_R \times \left( \frac{1}{R_2} + \frac{1}{R_3} \right) = \frac{V_A}{R_2} + \frac{V_O}{R_3} \rightarrow V_R \times \left( \frac{R_2 + R_3}{R_2 R_3} \right) = \frac{V_A}{R_2} + \frac{V_O}{R_3} \rightarrow V_R = V_A \frac{R_3}{R_2 + R_3} + V_O \frac{R_2}{R_2 + R_3}$$

1. Assume  $t = T_1^-$ ,  $V_A = L_-$ ,  $V_R = 0^-$ ,  $V_{C1} \uparrow$ ,

$$2. t = T_1, V_A = L_+, V_R = 0 \rightarrow 0 = V_A \frac{R_3}{R_2 + R_3} + V_O \frac{R_2}{R_2 + R_3} \rightarrow V_O = -V_A \frac{R_3}{R_2} = L_- \frac{R_3}{R_2}$$

3. Assume  $t = T_2^-$ ,  $V_A = L_+$ ,  $V_R = 0^+$ ,  $V_{C_1} \downarrow$ ,

4.  $t = T_2$ ,  $V_A = L_-$ ,  $V_R = 0$ ,  $\rightarrow 0 = V_A \frac{R_3}{R_2 + R_3} + V_O \frac{R_2}{R_2 + R_3} \rightarrow V_O = -V_A \frac{R_3}{R_2} = -L \frac{R_3}{R_2}$

Oscillation condition:  $R_2 > R_3$ .

Otherwise if  $V_R = 0^-$ ,  $V_A = -L$ ,  $V_O = -V_A \frac{R_3}{R_2} = -V_A = L$ , and next moment  $V_R = 0^+$ ,

$V_A = L = V_O$ , the capacitor  $C$  will not be able to charged.

## Components and Instrumentation


| Instrument     | Quantity | Components           | Quantity       |
|----------------|----------|----------------------|----------------|
| Oscilloscope   | 1        | $\mu A$ 741 (OP-Amp) | 2              |
| Multi-meter    | 1        | 1N 4001 (Diode)      | 2              |
| Power supplier | 2        | Resistance           | Designed value |
| Function Gen.  | 1        | Capacitance          | Designed value |

## Instrument confirmation

Before you proceed to any part of the experiment, please remember to do the **Instrument Examinations** to the instruments before performing any experiment. The examining procedures are shown in experiment 1.
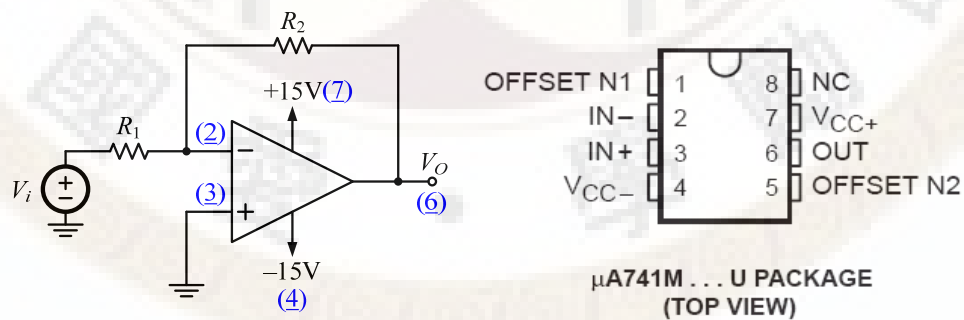
## Components confirmation

$\mu A741$  – PINOUT & Functional confirmation



$$\text{Check 1. } A_v = \frac{V_o}{V_i} = -\left(\frac{R_2}{R_1}\right)$$

$$\text{Check 2. } f_{3dB} = 100kHz \sim 500kHz$$

**Note:** Recall the expression of gain—bandwidth product:  $A_V \times f_{3dB} = \text{constant}$ , that is,  $f_{3dB}$  will reduce as  $A_V$  increases. If the results of confirmation appear the same as those shown in check 1 and 2, the  $\mu A741$  chip of OP amp is workable.

## Lab Work

### 1. Sinusoidal oscillators: Wien-bridge oscillator

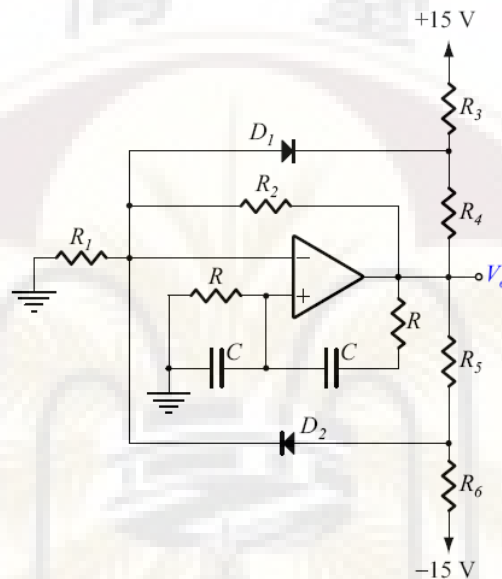


Fig. 3 Wien-bridge oscillator sinusoidal generator

#### Step 1. Without amplitude stabilization

- (1) In Fig. 3, disconnect  $D_1$ ,  $D_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ , and  $R_6$ .
- (2) Use  $R_1 = 3.3 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,
- (3) Oscilloscope ► Press the **DISPLAY** button ► **Format** ► **YT mode**.
- (4) Oscilloscope ► Press the **Measure** button ► Observe  $V_{\text{out (p-p)}}$  in CH1.
- (5) Record  $V_{\text{out (p-p)}} = \underline{\hspace{2cm}} \text{ V}$ ,  $f = \underline{\hspace{2cm}} \text{ Hz}$ .

#### Step 2. With amplitude stabilization

- (1) In Fig. 3, connect  $D_1$ ,  $D_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ , and  $R_6$ .
- (2) Use  $R_1 = 3.3 \text{ k}\Omega$ ,  $\text{VR}(R_2) = 10 \text{ k}\Omega$ ,
- (3) Oscilloscope ► Press the **DISPLAY** button ► **Format** ► **YT mode**.
- (4) Oscilloscope ► Press the **Measure** button ► Observe  $V_{\text{out (p-p)}}$  in CH1.
- (5) Adjust  $\text{VR}(R_2)$  until the sinusoidal vibration with the *minimum amplitude*

occurs in  $V_{out}$ .

(6) Record  $V_{out(p-p)} = \underline{\hspace{2cm}} \text{ V}$ ,  $f = \underline{\hspace{2cm}} \text{ Hz}$ ,  $R_2 = \underline{\hspace{2cm}} \text{ k}\Omega$ .

(7)  $R_2 / R_1 = \underline{\hspace{2cm}}$ .

(8) Adjust VR( $R_2$ ) until the sinusoidal vibration with the *maximum amplitude* occurs in  $V_{out}$ .

(9) Record  $V_{out(p-p)} = \underline{\hspace{2cm}} \text{ V}$ ,  $f = \underline{\hspace{2cm}} \text{ Hz}$ ,  $R_2 = \underline{\hspace{2cm}} \text{ k}\Omega$ .

(10)  $R_2 / R_1 = \underline{\hspace{2cm}}$ .

## 2. Sinusoidal oscillators: Phase-shift oscillator

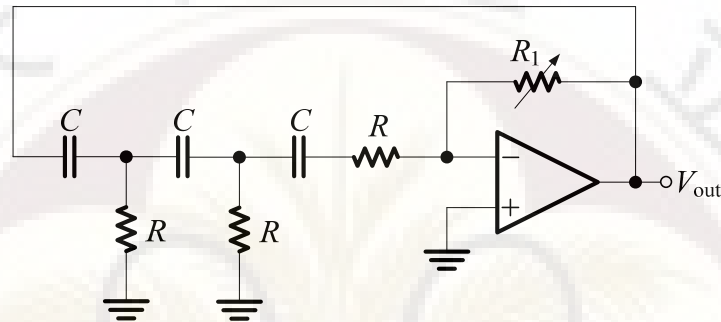


Fig. 4 Phase-shift oscillator sinusoidal generator

(1) In Fig. 4, use the designed value from Pre-Lab Work for components.

(2) Oscilloscope ► Press the **DISPLAY** button ► **Format** ► **YT mode**.

(3) Oscilloscope ► Press the **Measure** button ► Observe  $V_{out(p-p)}$  in CH1.

(4) Adjust VR ( $R_1$ ) until the sinusoidal vibration with the *minimum amplitude* occurs in  $V_O$ ,

(5) Record  $V_{out(p-p)} = \underline{\hspace{2cm}} \text{ V}$ ,  $f = \underline{\hspace{2cm}} \text{ Hz}$ ,  $R_1 = \underline{\hspace{2cm}} \text{ k}\Omega$ .

(6)  $R_1 / R = \underline{\hspace{2cm}}$ .

(7) Adjust VR ( $R_1$ ) until the sinusoidal vibration with the *maximum amplitude* occurs in  $V_O$ ,

(8) Record  $V_{out(p-p)} = \underline{\hspace{2cm}} \text{ V}$ ,  $f = \underline{\hspace{2cm}} \text{ Hz}$ ,  $R_1 = \underline{\hspace{2cm}} \text{ k}\Omega$ .

(9)  $R_1 / R = \underline{\hspace{2cm}}$ .



### 3. Triangular waveform generator: RC-circuit bistable multivibrator

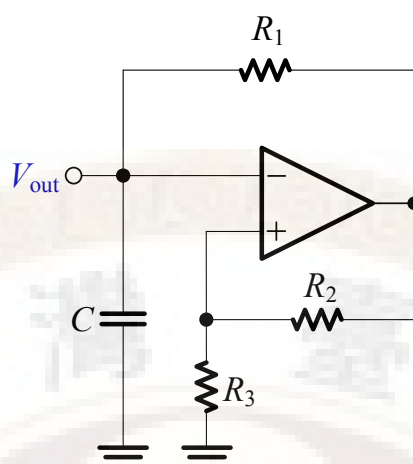


Fig. 5 RC-circuit Triangular waveform generator

- (1) In Fig. 5, use the designed value from PR (預報) for components.
- (2) Oscilloscope ► Press the **DISPLAY** button ► **Format** ► **YT mode**.
- (3) Oscilloscope ► Press the **Measure** button ► Observe  $V_{out(p-p)}$  in CH1.
- (4) Record  $V_{out(p-p)} = \underline{\hspace{2cm}}$  V,  $f = \underline{\hspace{2cm}}$  Hz.
- (5)  $R_1 = \underline{\hspace{2cm}}$  k $\Omega$ ,  $R_2 = \underline{\hspace{2cm}}$  k $\Omega$ ,  $R_3 = \underline{\hspace{2cm}}$  k $\Omega$ ,  $C = \underline{\hspace{2cm}}$  F.

### 4. Triangular waveform generator: Integrator bistable multivibrator

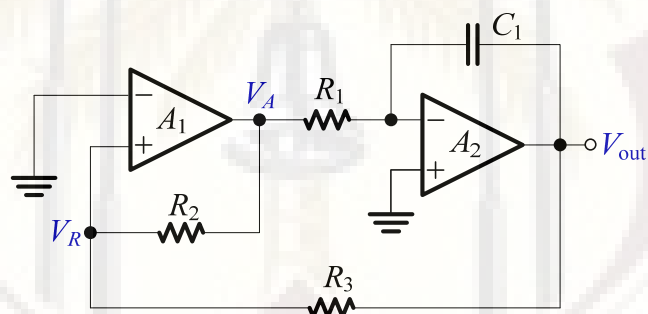


Fig. 6 Integrator bistable multivibrator

- (1) In Fig. 6, use the designed value from PR (預報) for components.  
**Note:** Choose  $R_2$  slightly greater  $R_3$  rather than identity.
- (2) Oscilloscope ► Press the **DISPLAY** button ► **Format** ► **YT mode**.
- (3) Oscilloscope ► Press the **Measure** button ► Observe  $V_{out(p-p)}$  in CH1.
- (4) Record  $V_{out(p-p)} = \underline{\hspace{2cm}}$  V,  $f = \underline{\hspace{2cm}}$  Hz,
- (5) Record  $R_2 = \underline{\hspace{2cm}}$  k $\Omega$ ,  $R_3 = \underline{\hspace{2cm}}$  k $\Omega$ .

## Reference

1. A.S. Sedra and K.C. Smith, *Microelectronic Circuits*, 6th ed., Oxford University Press publishing, New York, 2011.
2. A.S. Sedra and K.C. Smith, *Laboratory Manual for Microelectronic Circuits*, 3<sup>rd</sup> ed., Oxford University Press publishing, New York, 1997.