

Experiment 6 : Oscillators

Department : 電機三

Name : 楊正彥

Student ID : b03901086

Class Number : 三早

1. Experiment Objectives

1.1. Be familiar with the Barkhausen criterion and various kinds of oscillators.

2. Experiment Setups

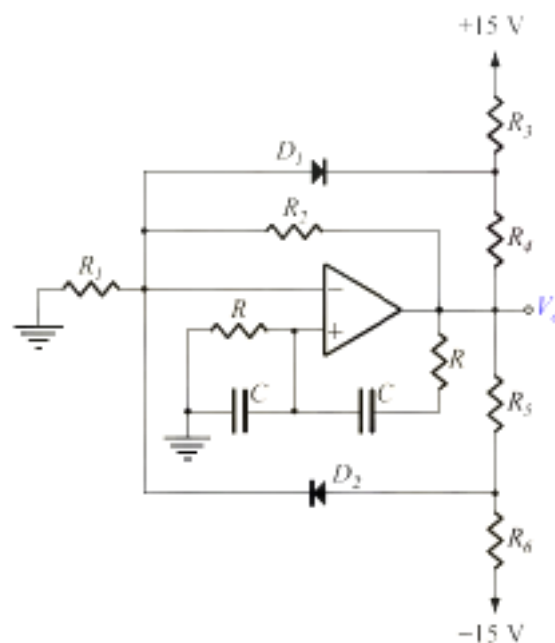


Fig. 3 Wien-bridge oscillator sinusoidal generator

1. Disconnect D_1 , D_2 , R_3 , R_4 , R_5 and R_6 , use $R_1 = 3.3k\Omega$ and $R_2 = 10k\Omega$.
2. Then tune to YT mode to observe the V_{out} .
3. Connect D_1 , D_2 , R_3 , R_4 , R_5 and R_6 , use $R_1 = 3.3k\Omega$ and $R_2 = 10k\Omega$.
4. Adjust the VR(R_2) until the sinusoidal vibration with the minimum amplitude occurs in V_{out} .
5. Then record the V_{out} , frequency and R_2 of the circuit.
6. Adjust the VR(R_2) until the sinusoidal vibration with the maximum amplitude occurs in V_{out} .
7. Again, record the V_{out} , frequency and R_2 of the circuit.